

# Flip-flops & Race-around Problems

Farhan Tanvir

1805073

Shehabul Islam Sawraz

1805088

Department of Computer Science and Engineering  
Bangladesh University of Engineering and Technology

August 29, 2022

# Table of Contents

- 1 Introduction
- 2 Types
- 3 Truth Table
- 4 Circuit Diagram
- 5 Misconception
- 6 Solution

# Checkpoint

- 1 Introduction
- 2 Types
- 3 Truth Table
- 4 Circuit Diagram
- 5 Misconception
- 6 Solution

# Before We Start!!!

- Before we dive into the discussions of Flip-flops, let's go for a quick introduction of it!
- And for that, we will need to know about one important concept first!

# Before We Start!!!

- Before we dive into the discussions of Flip-flops, let's go for a quick introduction of it!
- And for that, we will need to know about one important concept first!

# Sequential Circuits

- We know, pretty much in everywhere, output depends on input.

# Sequential Circuits

- We know, pretty much in everywhere, output depends on input.
- Putting it more formally in case of circuits... present output depends on present input.

# Sequential Circuits

- We know, pretty much in everywhere, output depends on input.
- Putting it more formally in case of circuits... present output depends on present input.
- **But output of sequential circuits depend on past output too!!!**



# Sequential Circuits (contd.)

- That brings an important point: we need to **store** the past output somewhere.

# Sequential Circuits (contd.)

- That brings an important point: we need to **store** the past output somewhere.
- For that, we need storage devices.

# Sequential Circuits (contd.)

- That brings an important point: we need to **store** the past output somewhere.
- For that, we need storage devices.
- And here is where **Flip-flop** comes in play.

# Sequential Circuits (contd.)


- That brings an important point: we need to **store** the past output somewhere.
- For that, we need storage devices.
- And here is where **Flip-flop** comes in play.
- This whole thing is also known as **storing the state of our circuit**.

# Two Important Questions

- ① What does Flip-flop do?
  - It stores and updates the state of our circuit
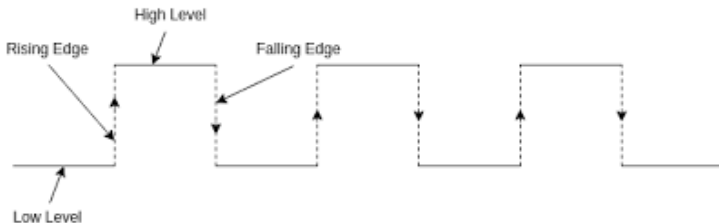
# Two Important Questions

- 1 What does Flip-flop do?
  - It stores and updates the state of our circuit
- 2 How does it know when to update the state?
  - It updates upon receiving a signal, whom we refer to as **clock**



# Checkpoint

1 Introduction

2 **Types**

3 Truth Table

4 Circuit Diagram

5 Misconception

6 Solution

# Types of Flip-flops

- SR (Set-Reset FF)
- D (Delay FF)
- T (Toggle FF)



# Types of Flip-flops

- SR (Set-Reset FF)
- D (Delay FF)
- T (Toggle FF)
- **JK (Jack Kilby FF)**

# Checkpoint

- 1 Introduction
- 2 Types
- 3 Truth Table**
- 4 Circuit Diagram
- 5 Misconception
- 6 Solution

# Truth Table for JK Flip-flop

J	K	$Q_{n-1}$	$Q_n$	Mode
0	0	0	0	Hold/Store
0	0	1	1	
0	1	0	0	Reset
0	1	1	0	
1	0	0	1	Set
1	0	1	1	
1	1	0	1	Toggle
1	1	1	0	

# Truth Table for JK Flip-flop

J	K	$Q_{n-1}$	$Q_n$	Mode
0	0	0	0	Hold/Store
0	0	1	1	
0	1	0	0	Reset
0	1	1	0	
1	0	0	1	Set
1	0	1	1	
1	1	0	1	Toggle
1	1	1	0	

# Truth Table for JK Flip-flop

J	K	$Q_{n-1}$	$Q_n$	Mode
0	0	0	0	Hold/Store
0	0	1	1	
0	1	0	0	Reset
0	1	1	0	
1	0	0	1	Set
1	0	1	1	
1	1	0	1	Toggle
1	1	1	0	

# Truth Table for JK Flip-flop

J	K	$Q_{n-1}$	$Q_n$	Mode
0	0	0	0	Hold/Store
0	0	1	1	
0	1	0	0	Reset
0	1	1	0	
1	0	0	1	Set
1	0	1	1	
1	1	0	1	Toggle
1	1	1	0	

# Some Trouble Waiting?

**When  $J = K = 1$ , an interesting event may occur depending on the clock mechanism. This event is known as Race Around Condition**




# Some Trouble Waiting?

When  $J = K = 1$ , an interesting event may occur depending on the clock mechanism. This event is known as **Race Around Condition**


# Checkpoint

- 1 Introduction
- 2 Types
- 3 Truth Table
- 4 Circuit Diagram**
- 5 Misconception
- 6 Solution


# Circuit Diagram for $J = K = 1$

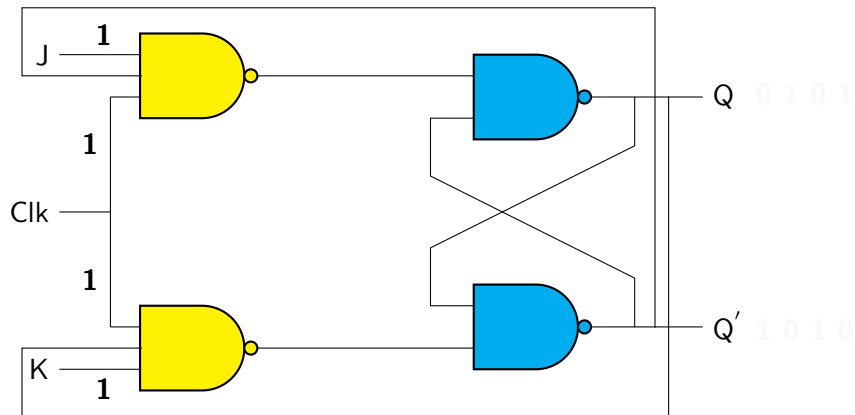


# Circuit Diagram for $J = K = 1$

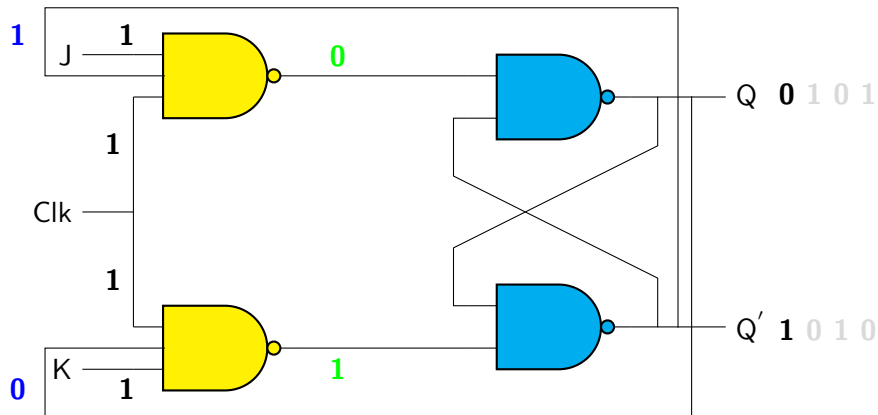


# Circuit Diagram for $J = K = 1$

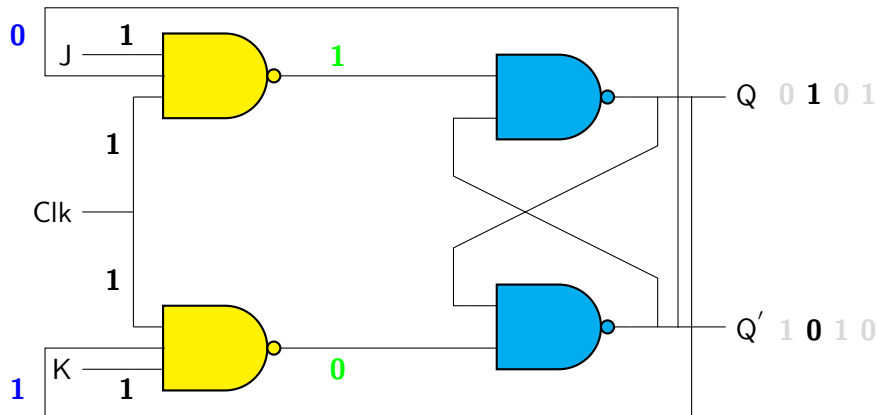

# Circuit Diagram for $J = K = 1$

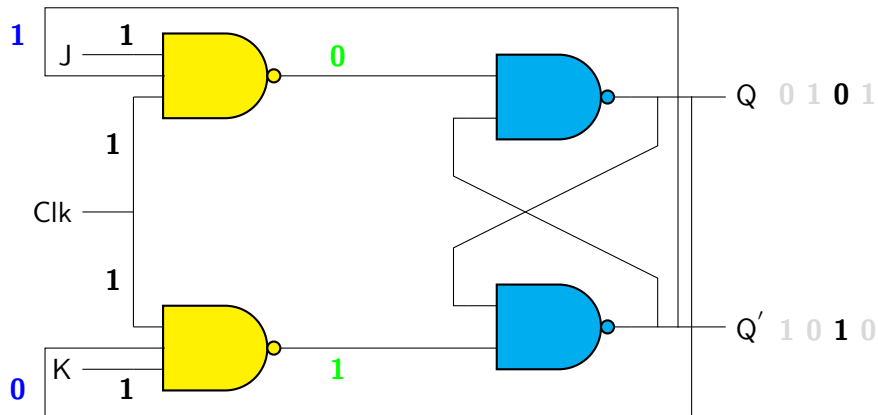

# Circuit Diagram for $J = K = 1$

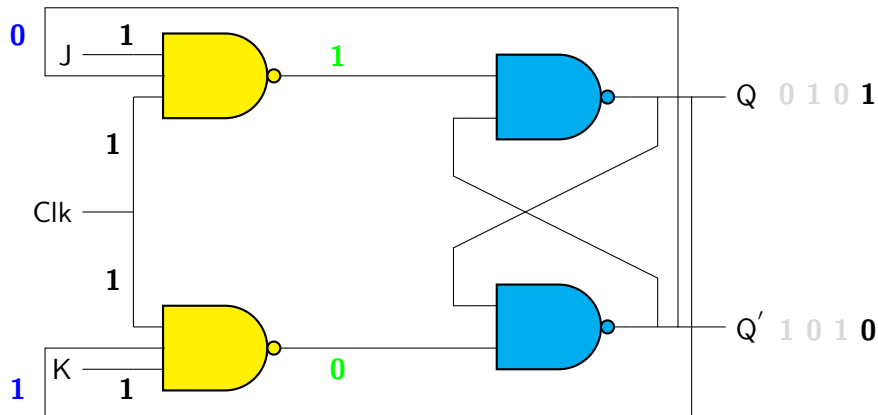

# Checkpoint

- 1 Introduction
- 2 Types
- 3 Truth Table
- 4 Circuit Diagram
- 5 Misconception**
- 6 Solution



# Some Misconception!!

## Fallacy


Toggling & Race Condition is same

# Checkpoint

- 1 Introduction
- 2 Types
- 3 Truth Table
- 4 Circuit Diagram
- 5 Misconception
- 6 Solution**
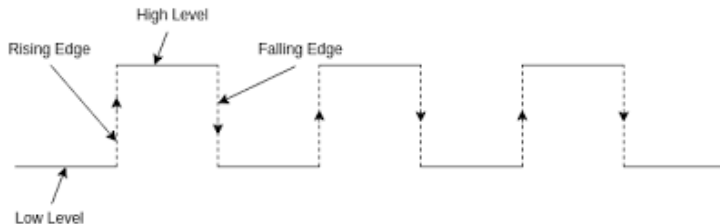
# Solution


- 1 Use edge triggering instead of level triggering



- 2 Use Master-Slave JK Flip-Flop
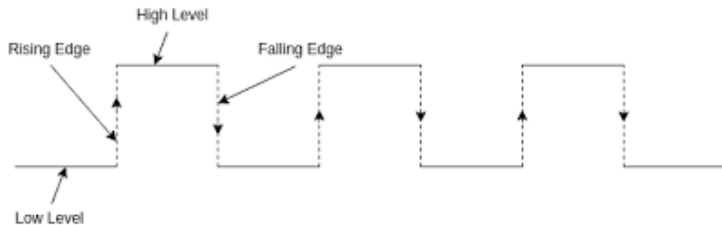
# Solution

- 1 Use edge triggering instead of level triggering



- 2 Use Master-Slave JK Flip-Flop